

明新科技大學 101 學年度研究所考試入學招生 試題卷

系所類別	科目	節次	准考證號碼 (考生請填入)	考試日期
電機工程系碩士班 (電機組)	電子學	第一節		101/4/29

※答案須寫在答案卷內，否則不予計分。

1. For the circuit shown in Fig. 1, assume that the diode with constant forward voltage drop $V_D=0.7V$. The circuit parameters are $V_{DD}=5V$ and $R=1k\Omega$. If the dissipated powers of diode and resistor are named P_D and P_R respectively. Determine the values of P_D and P_R . (10%)

 


Fig. 1

2. Considering the circuit shown in Fig. 2, assume that the operational amplifier is ideal. Derive the transfer function $A_V(S)=V_O(S)/V_i(S)$. (10%)

 


Fig. 2

 


Fig. 3

明新科技大學 101 學年度研究所考試入學招生 試題卷

系所類別	科目	節次	准考證號碼 (考生請填入)	考試日期
電機工程系碩士班 (電機組)	電子學	第一節		101/4/29

4. The operational amplifier circuit shown in Fig. 4 is a hysteresis comparator circuit. Assume that the operational amplifier is ideal and has the output saturation voltages $\pm 10V$. Derive and plot the transfer characteristics between v_o and v_i . (10%)
5. For the circuit shown in Fig. 5, assume that the NPN transistor has $\beta = 100$ and forward bias $V_{BE} = 0.7V$. Find the values of I_C , I_E , V_B , V_C , and V_E . (10%)

 


Fig. 4

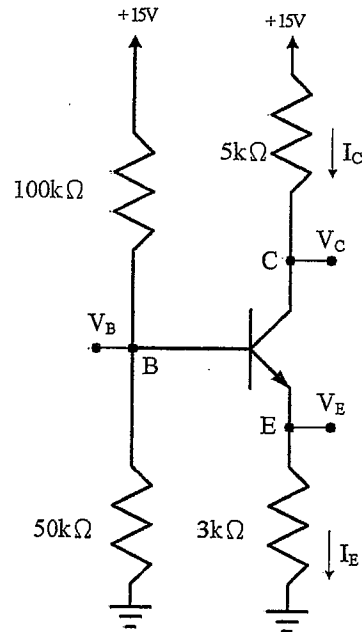


Fig. 5

明新科技大學 101 學年度研究所考試入學招生 試題卷

系所類別	科目	節次	准考證號碼 (考生請填入)	考試 日期
電機工程系碩士班 (電機組)	電子學	第一節		101/4/29

6. The small-signal model of an NPN transistor and its amplifier circuit are shown in Fig. 6.

(10 %)

(1) Plot the small-signal model of the amplifier circuit. (Hint : Let the current source I be open circuit, the three capacitors be short circuit, and the power supply V_{CC} be grounded.)

(2) Derive the voltage gain $A_v = v_o / v_i$.

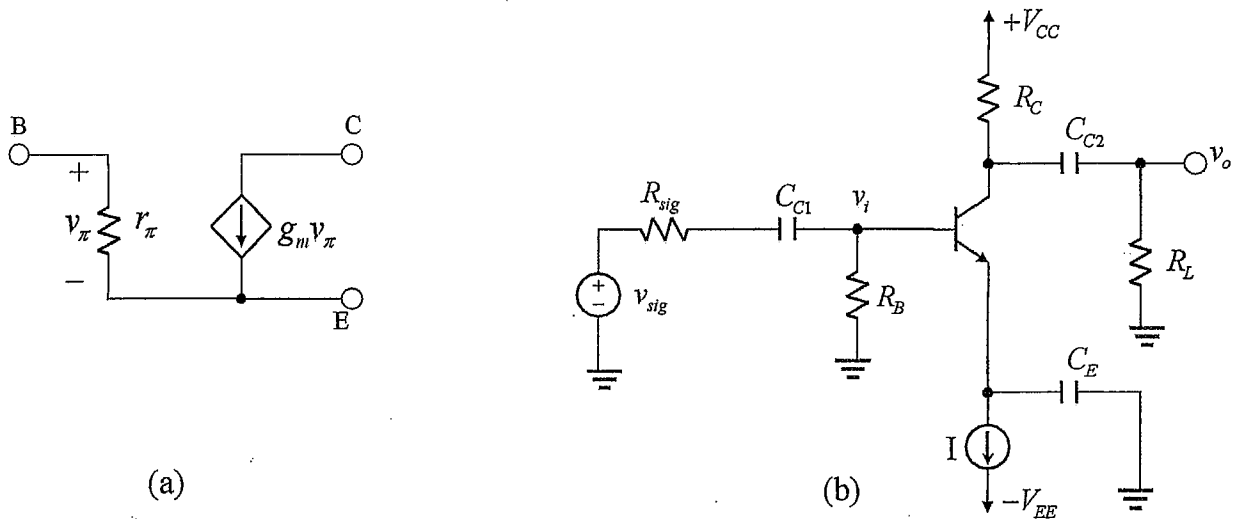


Fig. 6 (a) The small-signal model of an NPN transistor, (b) The NPN amplifier circuit.

明新科技大學 101 學年度研究所考試入學招生 試題卷

系所類別	科目	節次	准考證號碼 (考生請填入)	考試日期
電機工程系碩士班 (電機組)	電子學	第一節		101/4/29

7. The small-signal model of an NMOS transistor and its amplifier circuit are shown in Fig. 7.(10%)
- (1) Plot the small-signal model of the amplifier circuit. (Hint : Let the current source I be open circuit, the three capacitors be short circuit, and the power supply V_{DD} and V_{SS} be grounded.)
- (2) Derive the voltage gain $A_v = v_o / v_i$.

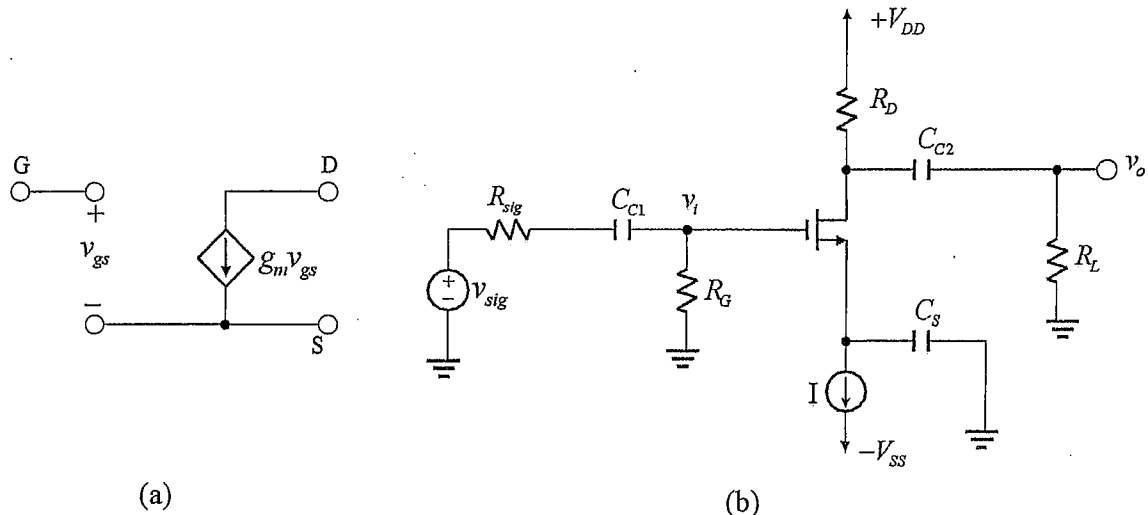


Fig. 7 (a) The small-signal model of an NMOS transistor, (b) The NMOS amplifier circuit.

8. A two-transistor current source (current mirror) is shown in Fig. 8. The current gain for both the transistor Q_1 and Q_2 is β , (a) Write down the expression of I_{REF} in terms of V^+, V^-, V_{BE}, R_1 , (b) Write down the relationship between I_O and I_{REF} . (10%)

 


Fig. 8 The current source (mirror) circuit.

明新科技大學 101 學年度研究所考試入學招生 試題卷

系所類別	科目	節次	准考證號碼 (考生請填入)	考試日期
電機工程系碩士班 (電機組)	電子學	第一節		101/4/29

9. A limiter circuit is shown in Fig. 9. The input signal is $v_I(t) = 10 \sin \omega t$. The breakdown voltage for the two zener diodes is $V_{Z1} = V_{Z2} = 8 \text{ V}$, The voltage drop for the two zener diodes when conducting in the forward direction is 0.7 V , $R = 10 \text{ K}\Omega$, Please plot the waveform of the output voltage v_O . (10 %)

 


Fig. 9 The limiter circuit and its input waveform.

10. A clamped capacitor (DC restorer) with a load resistance R is shown in Fig. 10. Assuming the diode is ideal, please plot the output waveform of the circuit with the square-wave input. (10 %)

 


Fig. 10 A clamped capacitor (DC restorer) with a load resistance R