

明新科技大學 102 學年度研究所考試入學招生 試題卷

系所類別	科目	節次	准考證號碼 (考生請填入)	考試日期
電機工程系碩士班 (電機組)	電子學	第一節		102/4/28

※答案須寫在答案卷內，否則不予計分。

- Assume that the diodes, in the forward bias condition, can be modeled as a constant voltage drop $V_D=0.7V$ in series with an equivalent resistance $r_D=20\Omega$. Design R and calculate I_D as shown in Fig. 1 to provide $V_o=1.6V$. (10%)
- Considering the ideal operational amplifier circuit shown in Fig. 2, find the expression of v_o in terms of v_1 and v_2 . (10%)

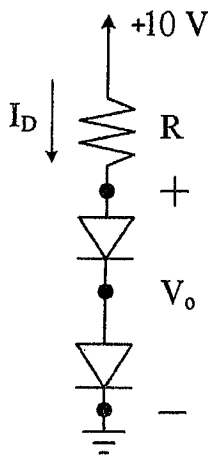


Fig. 1

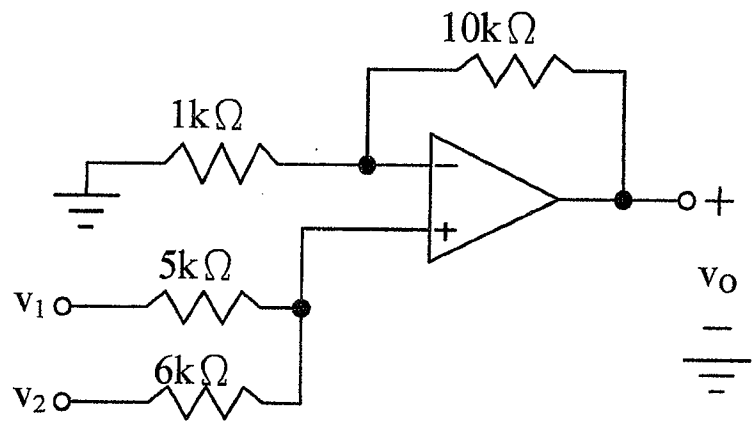


Fig. 2

- The inverting opamp circuit shown in Fig. 3 has output saturation voltages $=\pm 15V$. The other parameters of the opamp are assumed to be ideal and $R_1=10k\Omega$, $R_2=50k\Omega$.
 - When $V_i(t)=0.3\sin(2000\pi t)$, plot the waveform of $V_o(t)$ for at least one cycle. (5%)
 - When $V_i(t)=4\sin(2000\pi t)$, plot the waveform of $V_o(t)$ for at least one cycle. (5%)
- Fig. 4 is a simple opamp circuit with its output saturation voltages $=\pm 15V$ and differential voltage gain $A_v=10000(V/V)$. The other parameters of the opamp are assumed to be ideal.
 - When $V_i=1mV$, find the value of V_o . (5%)
 - When $V_i=100mV$, find the value of V_o . (5%)

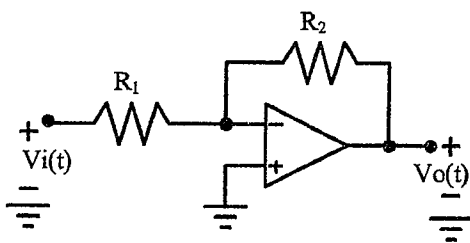


Fig. 3

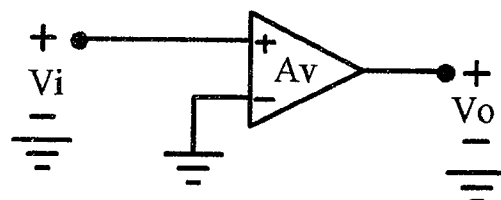


Fig. 4

明新科技大學 102 學年度研究所考試入學招生 試題卷

系所類別	科目	節次	准考證號碼 (考生請填入)	考試日期
電機工程系碩士班 (電機組)	電子學	第一節		102/4/28

5. For the circuit shown in Fig. 5, derive its transfer function $V_o(s)/V_i(s)$. If $R=1K\Omega$ and $C=0.1\mu F$, find its -3dB bandwidth $\omega_{BW}(\text{rad/sec})$ for the circuit. (10%)
6. For the circuit shown in Fig. 6, assume that NPN transistor has $\beta=50$ and BE forward bias voltage $V_{BE}=0.7V$. Find the values of I_C , I_E , V_B , V_C , and V_E . (10%)
7. Fig. 7 shows a simple NMOS circuit with $(\mu_n C_{ox})(W/L)=2\text{mA/V}^2$ and $V_{th}=1.0V$. Assume that an NMOS in saturation region has: $I_D=0.5(\mu_n C_{ox})(W/L)(V_{GS}-V_{th})^2$, and in triode region has: $I_D=(\mu_n C_{ox})(W/L)[(V_{GS}-V_{th})V_{DS}-0.5V_{DS}^2]$. When $V_G=1.5V$, determine the values of V_{GS} , and I_D . (10%)

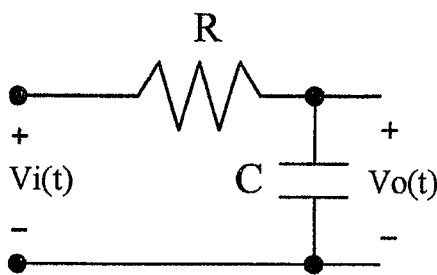


Fig. 5

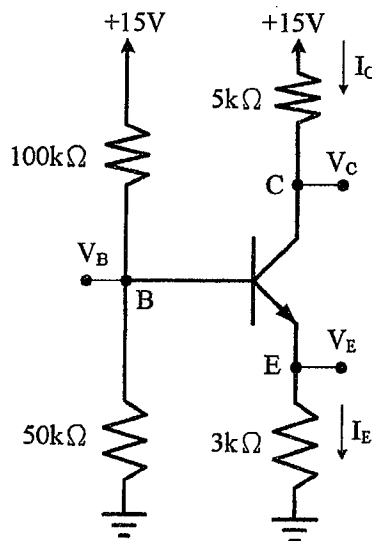


Fig. 6

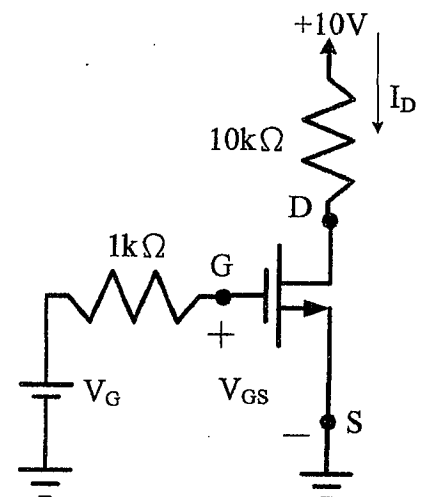


Fig. 7

明新科技大學 102 學年度研究所考試入學招生 試題卷

系所類別	科目	節次	准考證號碼 (考生請填入)	考試日期
電機工程系碩士班 (電機組)	電子學	第一節		102/4/28

8. For the current mirror circuit in Fig. 8 with $V_{DD}=V_{SS}=5V$, two enhancement NMOSFETs Q1 and Q2 have equal channel length and width with $(\mu_n C_{ox})(W/L)=1mA/V^2$ and $V_{th}=1.0V$. Assume that an NMOS in saturation region has $I_D=0.5(\mu_n C_{ox})(W/L)(V_{GS}-V_{th})^2$. Find the value of R to obtain $I_{D2}=0.5mA$ as Q2 operates in the saturation region. (10%)
9. According to the circuit shown in Fig. 9, the NMOSFET with $V_{th}=1.5V$ and $(\mu_n C_{ox})(W/L)=1mA/V^2$. If its small signal parameter $g_m=(\mu_n C_{ox})(W/L)(V_{GS}-V_{th})$, find the values of V_{GS} and g_m . (10%)
10. The Common Source amplifier shown in Fig. 10 is connected to a signal source v_{sig} with $R_{sig}=100k\Omega$ and a load resistance $R_L=15k\Omega$. Assume that the NMOSFET is properly biased in the saturation region and has the following small signal parameters $g_m=1mA/V$ and $r_o=150k\Omega$. Find the overall voltage gain $A_v=v_o/v_{sig}$. (10%)

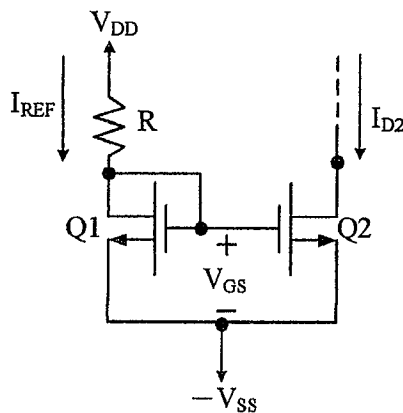


Fig. 8

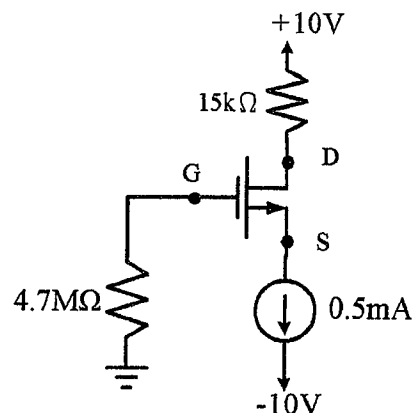


Fig. 9

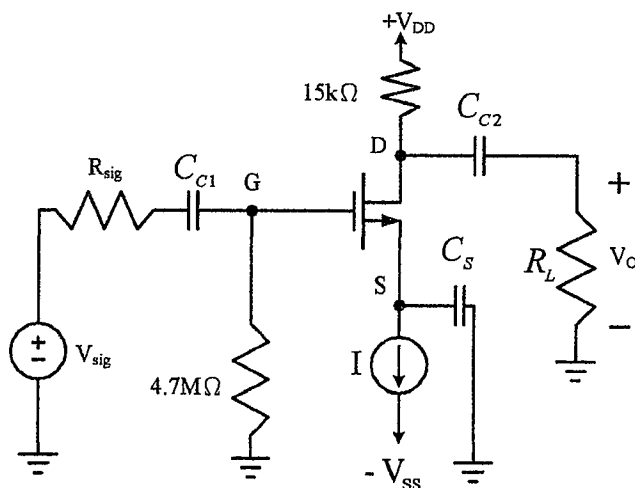


Fig. 10