

明新科技大學 105 學年度研究所考試入學招生 試題卷

系所類別	科目	節次	准考證號碼 (考生請填入)	考試 日期
電機工程系碩士班 (電機組)	電子學	第一節		105/4/24

※答案須寫在答案卷內，否則不予計分。

- In Fig. 1, assume that the diode with constant forward voltage drop  $0.7V$ . The circuit parameters are  $V_{DD}=10V$  and  $R=100\Omega$ . The dissipated powers of diode and resistor are  $P_D$  and  $P_R$  respectively. Calculate  $P_D$  and  $P_R$ . (Should you check the circuit carefully!)(10%)
- In Fig.2, each of the diodes can be modeled as a constant voltage drop  $V_D=0.7V$  in the forward biased region. If  $R=10\Omega$ , calculate the current  $I_D$  and the dissipated powers of  $R$ ,  $D1$ , and  $D2$  respectively. (10%)

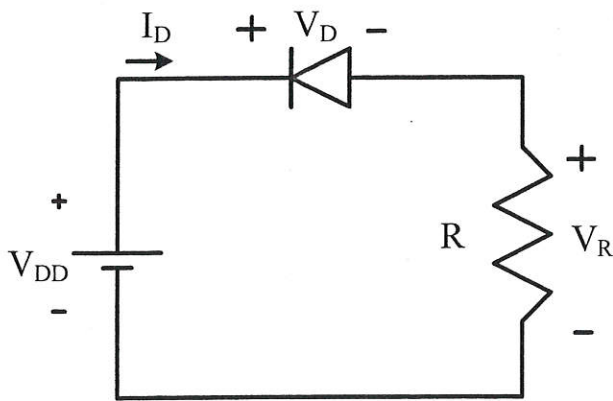


Fig. 1

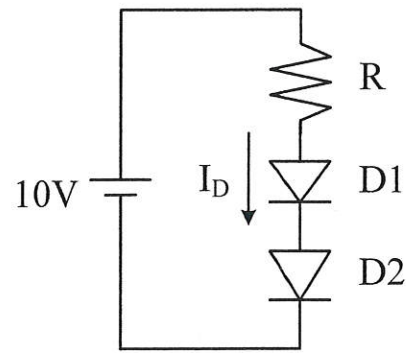


Fig. 2

- As reference to Fig. 3, assume that the op-amp is ideal. Derive the relationship between  $v_o$  and  $v_1, v_2, v_3$ . (10%)
- The op-amp circuit shown in Fig. 4 is a bi-stable circuit. The op-amp has output saturation voltages  $\pm 12V$ .
  - Derive and plot the transfer characteristics between  $v_o$  and  $v_i$ . (5%)
  - For  $R1=10k\Omega$ , find the value of  $R2$  to obtain threshold voltages of  $\pm 5V$  in this circuit. (5%)

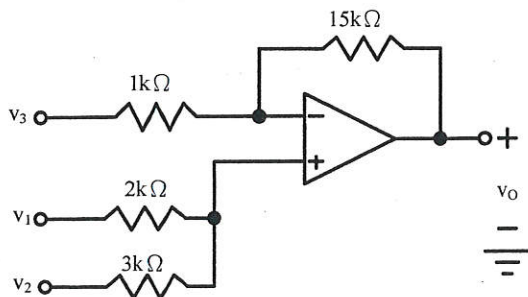


Fig. 3

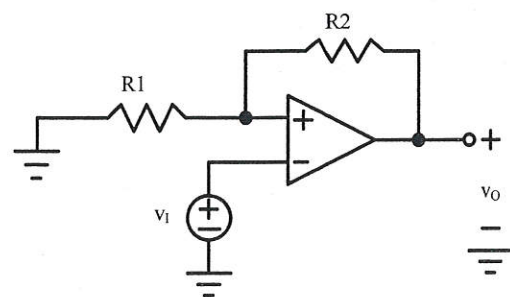


Fig. 4

5. For the circuit shown in Fig.5 is a RC single time constant circuit.  
 (A) Derive the transfer function  $T(S)=V_o(S)/V_i(S)$ . (5%)  
 (B) If  $R=10k\Omega$  and  $C=10\mu F$ , determine the bandwidth of this circuit. (5%)
6. For the circuit shown in Fig. 6, if  $R_1=1k\Omega$ ,  $R_2=10k\Omega$ , and  $C_2=4nF$ , derive an expression for the transfer function  $T(S)=V_o(S)/V_i(S)$  and find its DC gain and the -3dB frequency in Hz. (15%)

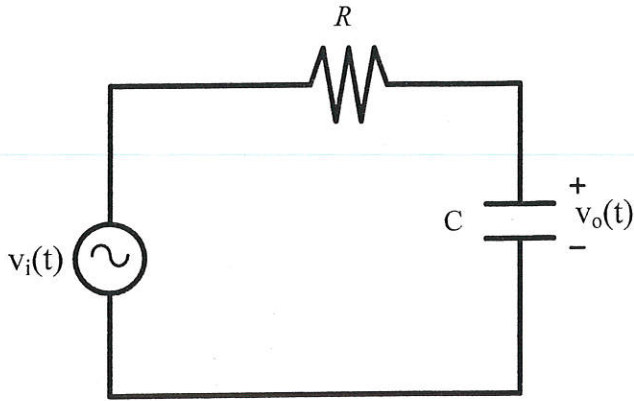


Fig. 5.

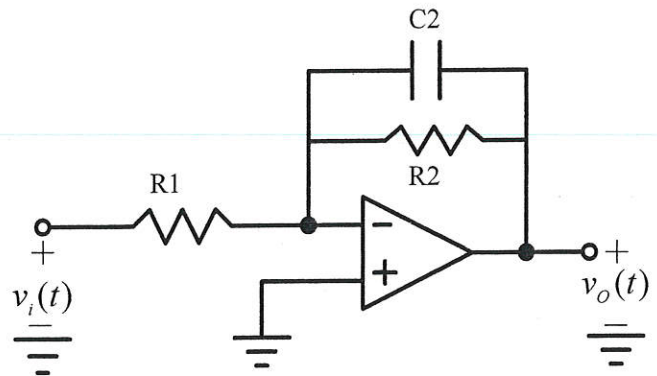


Fig. 6

7. Fig. 7 is a single stage N-MOSFET amplifier circuit. The N-MOSFET parameters are  $V_t=1.0V$ ,  $(\mu_n C_{ox})(W/L)=2mA/V^2$ ,  $V_A=100V$ .  
 (a) Determine its DC operating points of  $V_{GS}, V_G, I_D, V_D$ , and small signal parameters of  $g_m$  and  $r_o$ . (15%)  
 (b) Determine the small signal voltage gain of  $A_v=(v_o/v_{sig})$ . (10%)
8. Assume that the NPN transistor in Fig. 8 has  $\beta=100$  and  $V_{BE}=0.7V$ , calculate  $I_B, I_C, I_E, V_C$  and  $V_E$ . (10%)

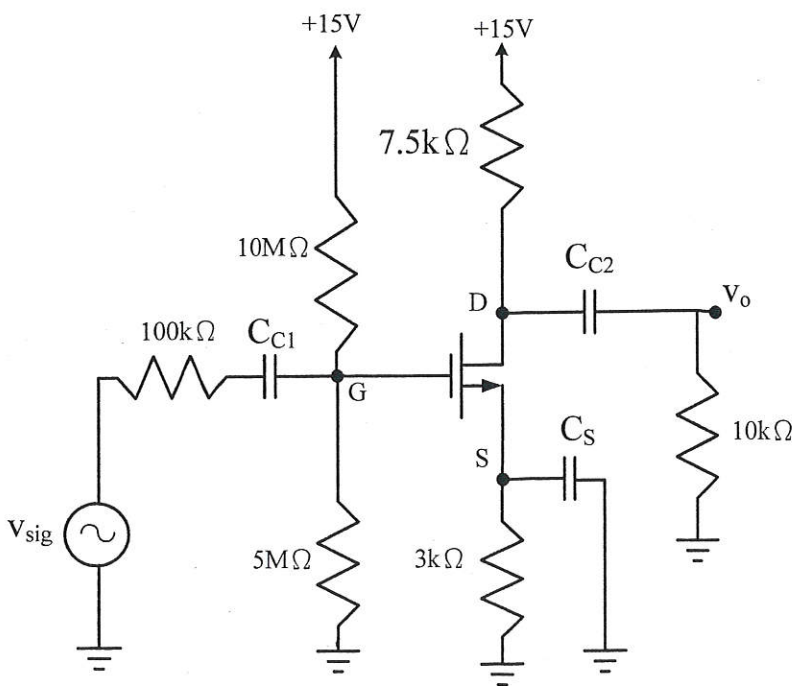


Fig. 7

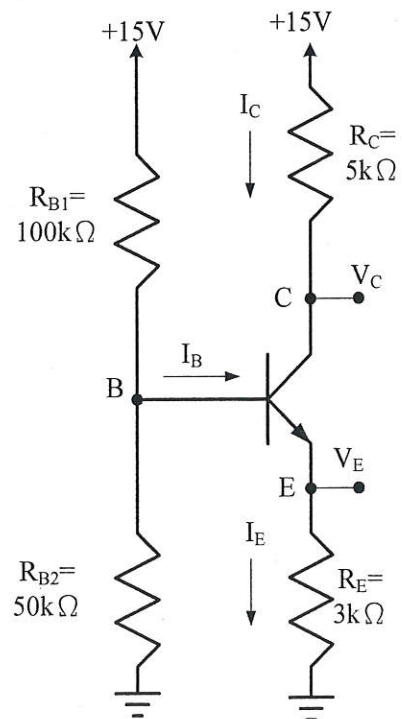


Fig. 8