
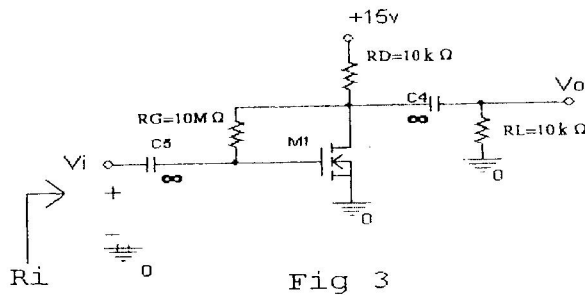
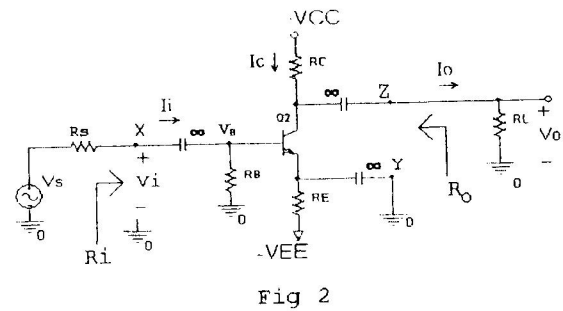


科目	考試日期	節次	准考證號碼
電子電路	92年5月11日	第2節	

- Assuming the op amp to be ideal, derive an expression for the close-loop gain v_o / v_i of the circuit in Fig.1. Use this circuit to design an inverting amplifier with a gain of 100 and input resistance of $1\text{M}\Omega$. Assume that for practical reasons it is required not to use resistor greater than $1\text{M}\Omega$. (Find the resistance R_1, R_2, R_3 , and R_4) (20%)
- For the circuit in Fig.2 let $R_B=100\text{k}\Omega, R_E=10\text{k}\Omega, R_C=10\text{k}\Omega, V_{CC}=V_{EE}=10\text{V}$, and let the BJT have $\beta=100$ and $V_A=100\text{V}$. (a) Find the values of V_B and I_C . (b) Find the values of the small signal model parameters g_m, r_π, r_e , and r_o at the bias point. (c) When connected in the common-emitter configuration with $R_S=R_1=10\text{k}\Omega$. Find the values of R_i, R_o, A_v, A_i . (Where $A_v \equiv v_o / v_s$ and $A_i \equiv i_o / i_i$) (20%)
- Fig.3 shows an enhancement MOSFET amplifier in which the output signal at the drain is coupled to the load resistance R_L via large capacitor. We wish to analyze this amplifier circuit to determine its small-signal voltage gain v_o / v_i and its input resistance R_i . The transistor has $V_t=1.5\text{V}, K=0.125\text{mA/V}^2$, and $V_A=50\text{V}$. (Hint: $V_t=V_p, K=I_{DSS}/V_p^2$) (20%)

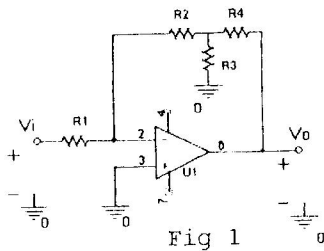

科目	考試日期	節次	准考證號碼
電子電路	92年5月11日	第2節	

4. For the ideal class B push-pull amplifier (Q1-Q2) in the Fig 4, $V_{cc}=20V, R_L=8\Omega$
 The input is sinusoidal. a. Determine the maximum output signal power. (5%),
 b. Determine the conversion efficiency (5%), c. The gain of the OP amplifier A is 50, $V_{be}=0.7V$, Sketch the transfer characteristic v_o versus v_i of the resulting feedback amplifier. (5%)

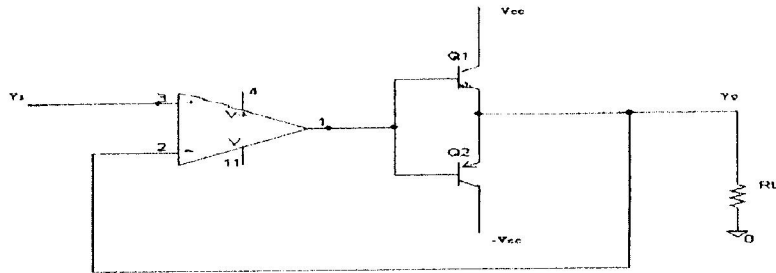


Fig. 4

5. a. Determine the frequency of the oscillation. (5%)
 b. Find the amplifier gain needed to just make this circuit oscillate. (5%)

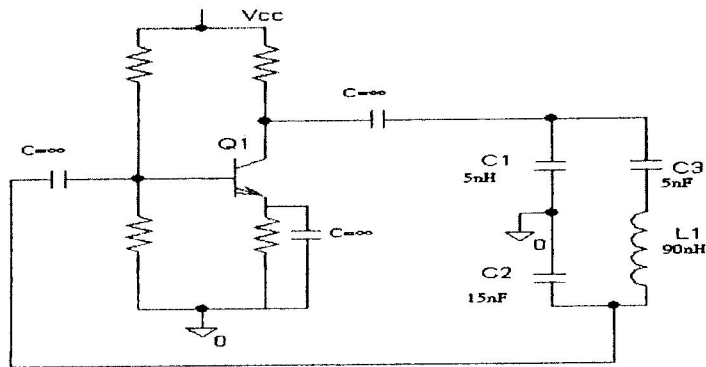


Fig. 5

6. Fig. 6a,6b are the first order active filters, $R_1=R_2=10k\Omega, C_1=1\mu F$
 a. What type of the filter is for the circuit shown in Fig. 6a,6b. (5%)
 b. Determine the transfer function v_o/v_i of the circuit by assuming the amplifier is an ideal OP amplifier. (10%)

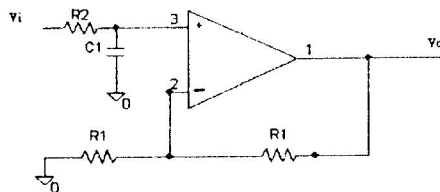


Fig 6a

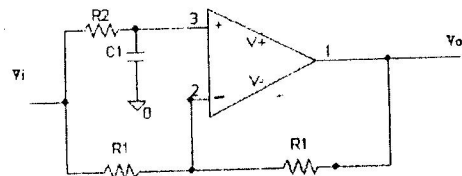


Fig. 6b