

系所別	組別	科目	考試日期	節次	時間
電機工程研究所		電子電路	93年5月2日	第二節	

1. The transistor amplifier in Fig. 1 is biased with a current source  $I$  and has  $\beta = 100$ . What is the voltage gain? (10%)

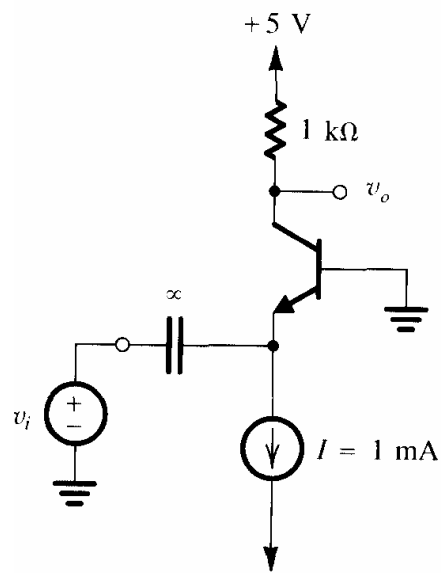


Fig. 1.

2. Consider the CMOS amplifier of Fig. 2 when fabricated with a technology for which  $W/L = 100\mu\text{m}/2\mu\text{m}$  for all transistors,  $k'_n = 100\mu\text{A}/\text{V}^2$ ,  $k'_p = 30\mu\text{A}/\text{V}^2$ ,  $I_{REF} = 100\mu\text{A}$ ,  $V_{An} = 8L(\mu\text{m})$ , volts and  $|V_{Ap}| = 12L(\mu\text{m})$ , volts. Find the voltage gain. (10%)

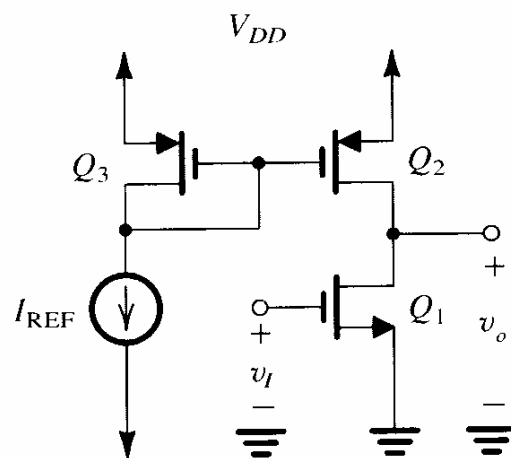


Fig. 2.

3. The amplifier in Fig. 3 is biased to operate at  $I_D = 1\text{mA}$  and  $g_m = 1\text{mA}/\text{V}$ . Neglecting  $r_o$ , find the value of  $C_s$  that places the corresponding pole at 20 Hz. What is the frequency of the transfer-function zero introduced by  $C_s$ ? (10%)

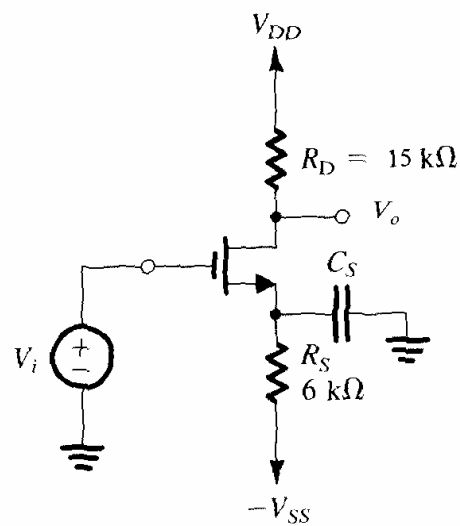


Fig. 3.

系所別	組別	科目	考試日期	節次	時間
電機工程研究所		電子電路	93年5月2日	第二節	

4. Consider the op amp-RC circuit shown in Fig. 4. We wish to use this circuit as a phase shifter. If the input signal frequency is  $10^3 \text{ rad/s}$  and if  $C = 10 \text{ nF}$ , find the value of R required to obtain phase shift of  $-60^\circ$ . (10%)

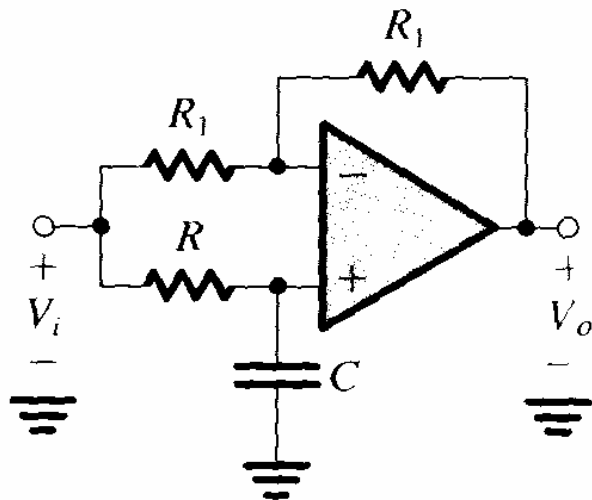


Fig. 4.

5. For the circuit shown in Fig. 5, both diodes are identical, conducting 10mA at 0.7V and 100mA at 0.8V. Find the value R, for which  $V=40\text{mV}$ . (10%)

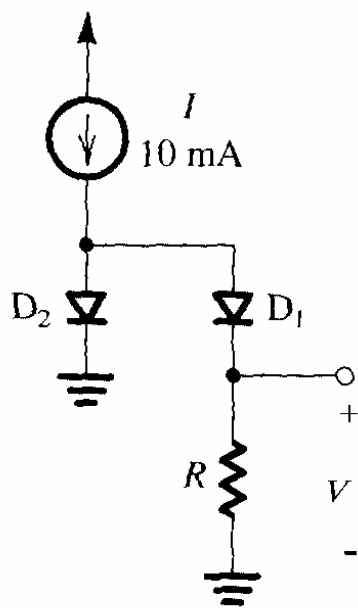


Fig. 5.

6. Determine the current I in the circuit shown in Fig. 6. (10%)

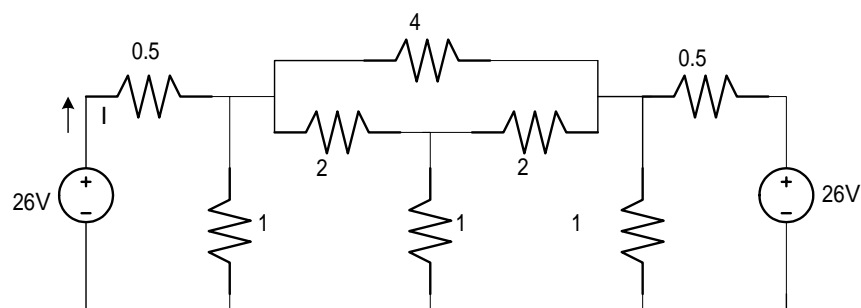


Fig. 6.

系所別	組別	科目	考試日期	節次	時間
電機工程研究所		電子電路	93年5月2日	第二節	

7. Find the Thevenin equivalent circuit of the network shown in Fig. 7. (10%)


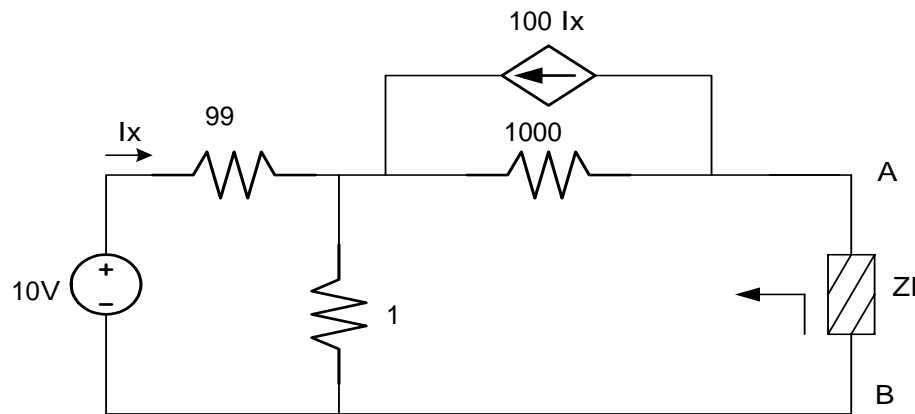


Fig. 7

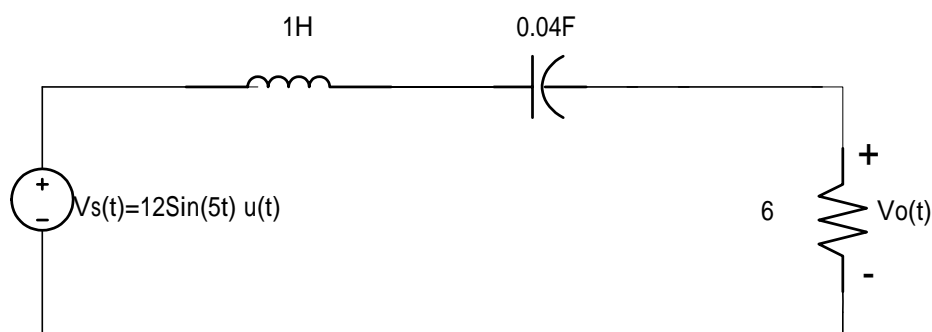8. For a circuit shown below, please find the zero state response  $V_o(t)$ . (10%)



9. The transfer function for a linear circuit is

$$H(s) = \frac{V_o}{I_i} = \frac{625(s+100)}{s^2 + 100s + 12500}$$

If  $i_i(t) = 4 \cos(50t + 60^\circ)$ , find the steady-state expression for  $V_o(t)$ . (10%)

10. Given the following voltage source

$$v_s(t) = 260\sqrt{2} \cos(\omega t)$$

together with a nonlinear load such that the resulting load current

$$i(t) = 100\sqrt{2} \cos(\omega t + 60^\circ) + 10\sqrt{2} \cos(3\omega t - 12^\circ) + 5\sqrt{2} \cos(5\omega t + 40^\circ) + 3\sqrt{2} \cos(7\omega t - 20^\circ)$$

Find the power factor of this load. (10%)