

系所類別	科目	節次	准考證號碼 (考生請填入)	考試日期
電機工程系碩士班 (電機組)	電子學	第一節		104/4/26

※答案須寫在答案卷內，否則不予計分。

1. In Fig. 1, assume that the diode with constant forward voltage drop $V_D=0.8V$. The circuit parameters are $V_{DD}=5V$ and $R=1k\Omega$. The dissipated powers of diode and resistor are P_D and P_R respectively. Calculate P_D and P_R . (10%)

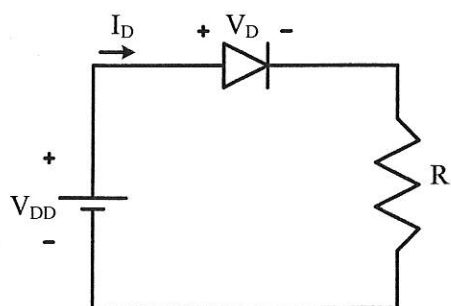


Fig. 1

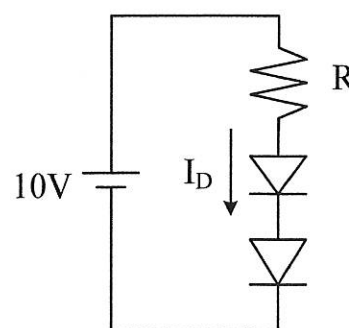


Fig. 2

3. According to the non-inverting op-amp circuit in Fig. 3, answer the following questions.

(a) What is the voltage gain of $A_v=(V_o/V_i)$? (5%)

(b) When $V_i=0.3\sin(2000\pi t)$, find V_o . (5%)

4. Fig. 4 is a simple op-amp circuit with its output saturation voltages $=\pm 15V$ and differential voltage gain $A_v=100000(V/V)$. The other parameters of the op-amp are assumed to be ideal.

(a) When $V_i=0.1mV$, find V_o . (5%)

(b) When $V_i=0.1V$, find V_o . (5%)

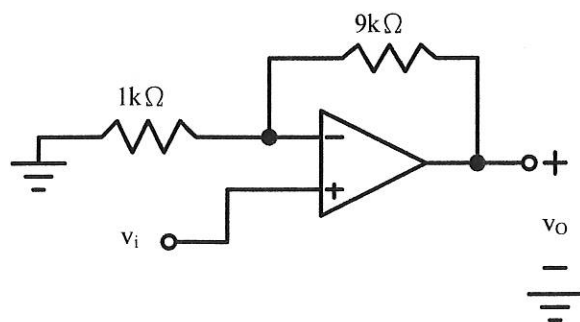


Fig. 3

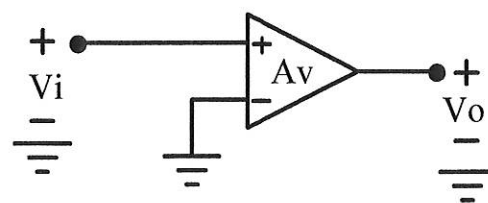


Fig. 4

系所類別	科目	節次	准考證號碼 (考生請填入)	考試日期
電機工程系碩士班 (電機組)	電子學	第一節		104/4/26

5. Fig. 5 is an inverting integrating circuit with its op-amp is ideal. Derive its voltage gain transfer function of $A_v(S)=V_o(S)/V_i(S)$. (10%)

6 Fig. 6 is an RC single time constant circuit. If $R=10k\Omega$ and $C=10\mu F$, find the transfer function $T(S)=V_o(S)/V_i(S)$. (10%)

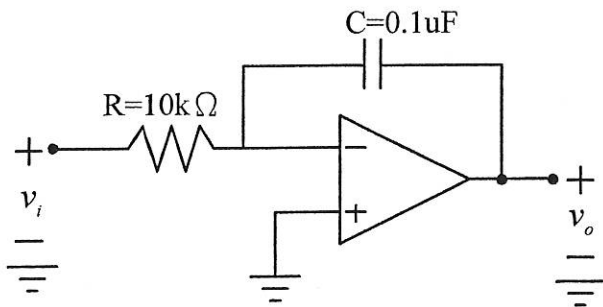


Fig. 5

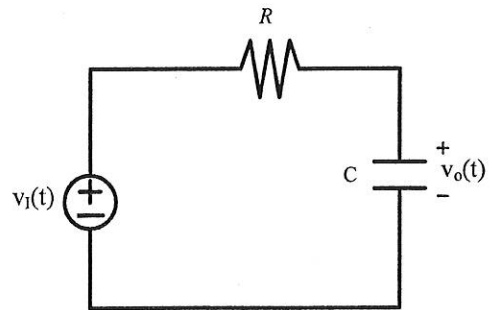


Fig. 6

7. In Fig. 7, assume that the operational amplifier is ideal. Find the voltage gain $A_v=v_o/v_i$. (10%)

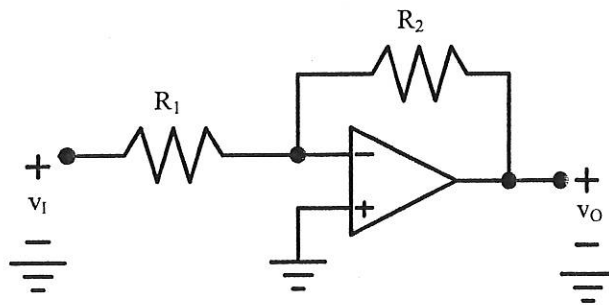


Fig. 7

系所類別	科目	節次	准考證號碼 (考生請填入)	考試日期
電機工程系碩士班 (電機組)	電子學	第一節		104/4/26

8. In Fig. 8, the NMOSFET has $V_t=1V$ and $(\mu_n C_{ox})(W/L)=1mA/V^2$. Find V_D and I_D . (10%)
9. In Fig. 9, the Common Source Amplifier is connected to a signal source v_{sig} with $R_{sig}=100k\Omega$ and a load resistance $R_L=15k\Omega$. Assume that the NMOSFET is properly biased in the saturation region and has the following parameters $g_m=1mA/V$. Find the overall voltage gain $A_v=v_o/v_{sig}$. (10%)

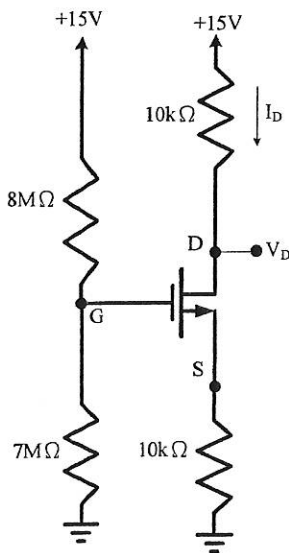


Fig. 8

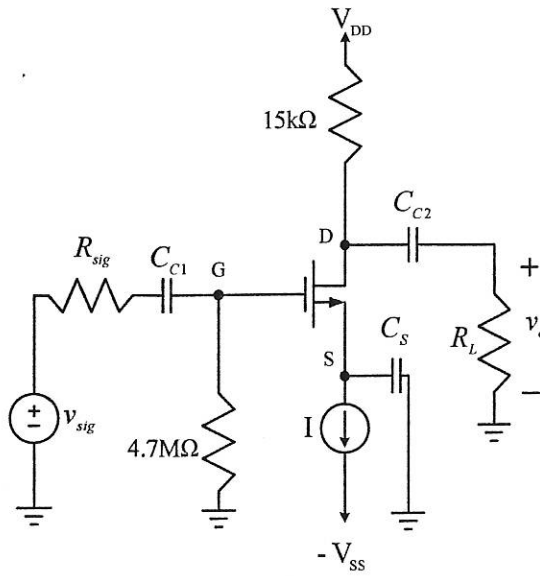


Fig. 9

10. In Fig. 10, assume the NPN transistor has $\beta=100$ and BE forward bias voltage $V_{BE}=0.7V$. Find I_B , I_C , I_E , and V_{CE} . (10%)

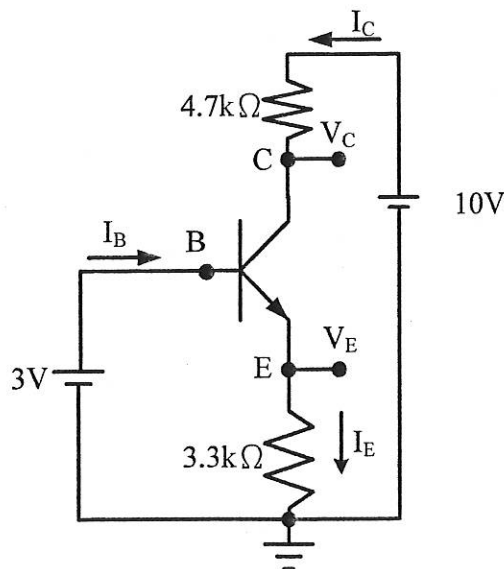


Fig. 10