

明新科技大學九十二學年度電子工程研究所招生

一般生電子學試題


1. An M-N flip-flop works as following table:

Present State Q	Next State Q ⁺	M	N
0	0	0	X
0	1	1	X
1	0	X	0
1	1	X	1

Using the above table and Karnaugh maps, derive and minimize the input equations for a counter composed of 3 M-N flip-flops which counts in the following sequence:


ABC= 000,001,011,111,101,100,000,... (20%)

 2. Sketch the output voltage(V_{OUT}) waveform in following OP-Amp circuit. (20%)




3. Calculate the built-in potential(V_{bi}) for a silicon p-n junction with $N_A=10^{19} \text{ cm}^{-3}$, $N_D=10^{15} \text{ cm}^{-3}$ at 300°K . ($n_i=9.65 \times 10^9 \text{ cm}^{-3}$) (15%)

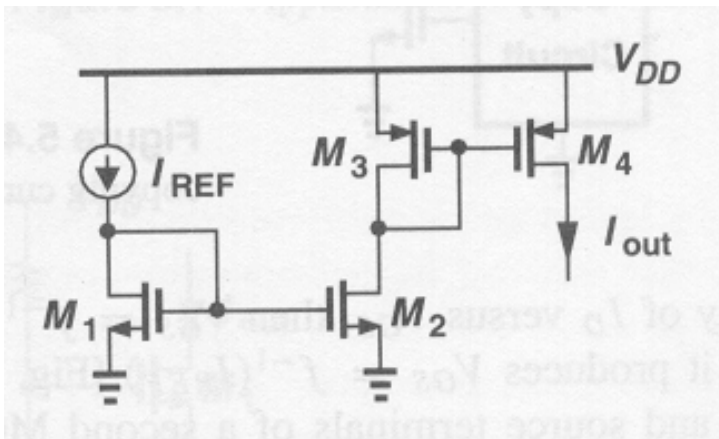4. Find the drain current of M_4 , given that $I_{ref} = 10 \mu\text{A}$, $(W/L)_1 = (2 \mu/1 \mu)$, $(W/L)_2 = (W/L)_3 = (4 \mu/1 \mu)$, and $(W/L)_4 = (8 \mu/0.5 \mu)$. (15%)



 5. Draw a high-frequency Bode-plot for the FET amplifier as below, $C_{iss}=8\text{pF}$, $C_{rss}=3\text{pF}$, $g_m=6500\mu\text{S}$.



(15%)

6. Given a HSPICE netlist, please draw the complete circuit diagram. (15%)

```
v1 vcc 0 dc 5v
m1 mout bs b vcc pfet W=3u L=0.6u
m2 b s mout 0 nfet W=1u L=0.6u
m3 mout s a vcc pfet W=3u L=0.6u
m4 a bs mout 0 nfet W=1u L=0.6u
xp s bs inv
.subckt inv in out
v1 vcc 0 dc 5v
m1 out in vcc vcc pfet W=3u L=0.6u
m2 out in 0 0 nfet W=1u L=0.6u
.ends
```

*****8